

### Procedure:

This lab focused on implementing algorithms as hardware circuits by utilizing Algorithmic State Machine and Datapath (ASMD) charts. ASMD charts such as Figure 1.1 allow the specification of digital systems such that specific hardware implementation can be communicated and thus implemented. Both tasks also focused on breaking down systems into its Datapath and Controller components. Task 1 comprised of creating an 8-bit bit-counting module based on a given ASMD chart that counted how many 1's were in a given input; the implementation was then to be tested and demonstrated on a DE1\_SoC board. Task 2 comprised of creating a binary search algorithm through utilization of a Memory Initialization File (MIF) by creating an ASMD chart for the binary search algorithm. Both tasks were then to be implemented and demonstrated on a DE1\_SoC board.

### Task 1: Bit-Counter

The goal of this task was to implement the bit-counting circuit in System Verilog using the ASMD chart shown below in Figure 1.1.

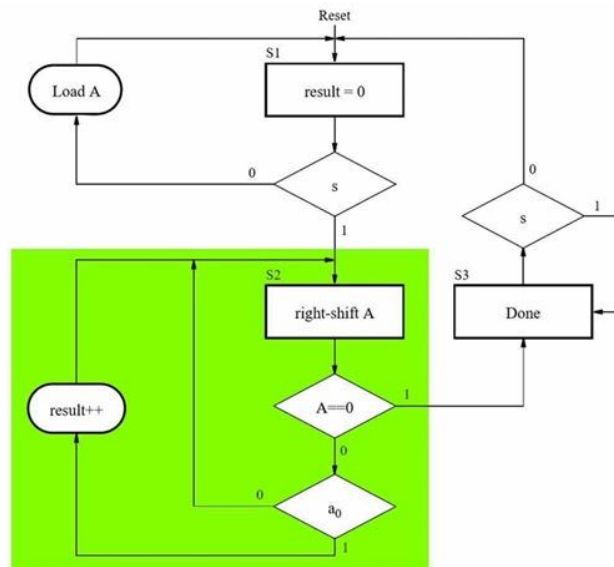


Figure 1.1: Bit-Counter ASMD Chart

The specification requests that all datapath components and an FSM within the control circuit are implemented as separate (sub)modules. The bit-counting system should then be implemented on the DE1\_SoC such that complete functionality can be tested. The specification specifically stated that `SW[7:0]` should correlate to the 8-bit input (`A`), `SW[9]` as the start signal (`s`), `KEY[0]` as the synchronous reset, and the 50 MHz clock signal (`CLOCK_50`) to drive the entire system. The functionality was then to be demonstrated on a DE1\_SoC video and recorded after all modules were tested.

### Task 2: Binary Search Algorithm

The goal of this task was to implement a binary search algorithm that searched through an array to locate a specified 8-bit value A. For the array to look for values in, this was implemented as a 32x8 RAM instantiated within Quartus using the methods learned in lab 2. First, an ASMD chart for the algorithm was to be created with the assumption that the array had a fixed size of 32 elements. Next, an FSM and datapath were to be implemented in SystemVerilog and then connected to a memory block. The algorithm was then to be implemented on the DE1 SoC board with the specifications of: SW9 as 'start', SW[7:0] to specify 'A', KEY0 for reset, CLOCK\_50 as the driving clock signal, HEX1 and HEX0 to display the address of data A in hex, and lastly LEDR9 for 'Found' and LEDR8 for 'Not Found'. For ease of testing and debugging, LED1 would indicate when the algorithm finished running and LED0 would light up when a reset signal was received. A MIF file called *my\_array.mif* was to be created and filled with an ordered set of 32 8-bit integer numbers. In this case, the MIF file simply held increasing integers 0 to 31, the value of the address number at each address. The functionality was then to be demonstrated on a DE1 SoC video and recorded after all modules are tested. Like the previous task, datapath and controls are to be separated into separate (sub)modules.

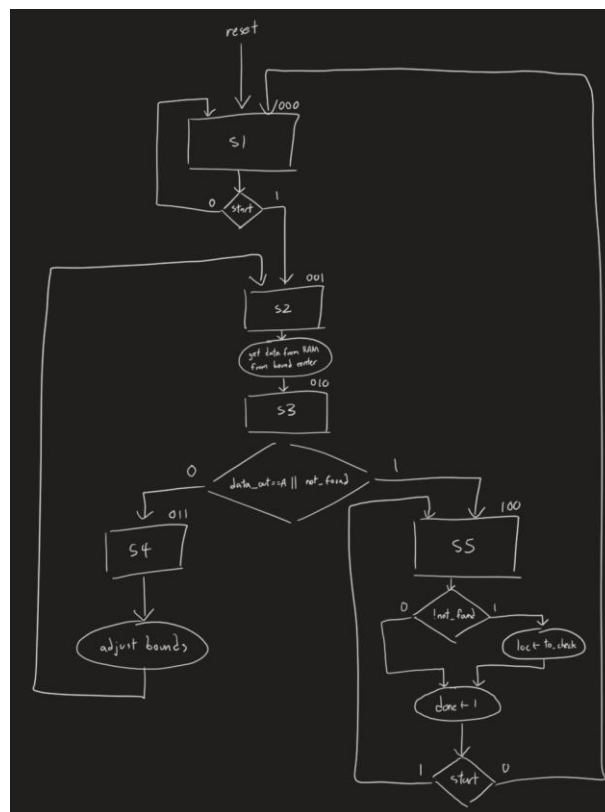


Figure 1.2: Binary Search ASMD Chart

## Results:

### Task 1: Bit-Counter

We approached the bit-counter by creating *bitCounter.sv* which served as the main bit-counting module that implemented the ASMD chart provided in Figure 1.1. This module included submodules *bitCounter\_datapath* which contained all datapath elements, *bitCounter\_controller* which contained the FSM and control signal operations and output, and three testbenches which tested the complete functionality, datapath functionality, and controller functionality of the *bitCounter* module. Although the code in a single file was very long, we decided that to keep it all under *bitCounter.sv* as it is more

intuitive and easier to use for other systems and projects; there also would not be much use for the controller and datapath as separate files too.

Parameters A\_WIDTH and RES\_WIDTH were used for code and module versatility, representing input A width and results width respectively which in this lab were set to 8 and 4 bits; 8 bits for the length of A, 4 bits to capture the maximum number of 1's in said input.

The bitCounter\_datapath module takes in a clock signal (clk) and all control signals outputted from bitCounter\_controller (incr\_result, rshift\_a, load\_A, reset\_result, done\_). The module then stores and performs all data operations given the inputted control signals, storing and outputting the updated A value for the control unit (A\_new), the total count of 1's in the input (result), and 'done' (status signal for bit-counting complete). The testbench tested all data manipulations and data storage by testing each control signal individually on a sample input data A and done signal. The waveform generated can be seen below:

 


Figure 1.3: bitCounter\_datapath Waveform

The waveform shows load\_A loading in the input A value provided, and reset\_result setting the resetting the result value to 0; both instantiation signals altered the data correctly. The result increments from 0 to 8 during when incr\_result is true, and resets to 0 when reset\_result is set to true; therefore the incrementing data works as intended. Next, rshift\_A successfully set A\_new to the input A shifted one value right, 8'b10101010 to 8'b01010101. Lastly, done reflects the input signal done\_, therefore showing that the datapath stores the done signal/value correctly. As an additional test, A\_new updates to new input A = 8'b11110000 when load\_A is set to 1 again, therefore the load signal is verified.

The bitCounter\_controller module takes in a clock (clk), reset, s (start signal), and input data 'A' which should be the output from the datapath as those values are updated. The module then utilizes a 3-state FSM and combinational as well as sequential logic to calculate and output control signals incr\_result (increment results by 1), rshift\_A (right shift A by 1), load\_A (load in new A value to system), reset\_result (initialize result to 0), and done\_ (done signal for datapath to store). The testbench tested all FSM transitions and tested sequences and combinations that outputted an output of 1 for each control signal. The waveform generated can be seen below:

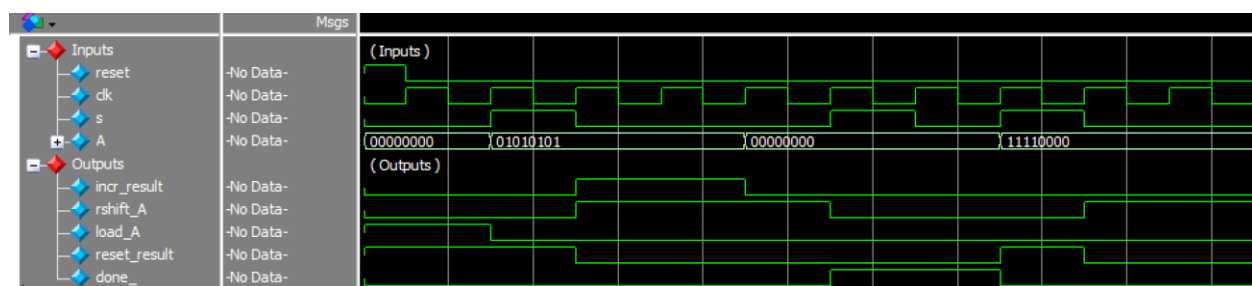


Figure 1.4: bitCounter\_controller Waveform

The waveform shows `reset_result` and `load_A` being active during initial state S1, which is the expected result as result must be reset to 0 and the data input A must be loaded at the start of the system. When start signal 's' is asserted, the FSM transitions into state S2 where the counting process begins. Since the least significant bit is 1 in state S2, the output signal `incr_result` and `rshift_A` are set to true, representing how the count of 1's (result) should increment, and the A value being analyzed must be shifted right as the right-most data has been analyzed already. When the rest of A is set to 0 while in S2, the FSM transitions into S3 as there are no more 1's left to possibly add to the results, therefore the count is finished. Since the count is finished, the `done` signal is set to 1, indicating the bit-counting is complete. Lastly, loading in a new value A (8'b00000000 since there wasn't a clock cycle to allow 8'b11110000 to be loaded) and resetting the system was tested by turning 's' off and on; the expected results similar to the first run are seen as `load_A` remained off, `reset_result` turned on, then the state transitioned to S2, and giving the signal that the data should be shifted right after analyzing the left-most bit of 0 which does not signify and incrementing result.

The bitCounter top module then instantiated the datapath and control submodules to cleanly implement the entire ASMD chart. A testbench 'bitCounter\_tb' was then created which tested all ASMD chart branches and functions. Notably, the test bench tested reset, changing input data without starting, then using the bitCounter system on 8'b00000001 to 8'b00000011 to 8'b00000111 . . . to 8'b11111111, then 8'b11111111 left shifted eventually to 8'b0. The waveform can be seen in the figure below:

 


Figure 1.5: bitCounter\_tb Waveform Part 1



Figure 1.6: bitCounter\_tb Waveform Part 2

Starting with the leftmost side of Figure 1.4, the testbench resets to initialize the system then tests if the actual bit-counting operation begins or does not begin without a start signal. The waveform depicts the expected functionality as 'result' and 'done' both remain at 0 until the start signal is provided later on. Throughout the rest of the waveform, the results can be seen settling to the total number of 1's contained in the input data A at the time when the start signal began; the done signal also reflects when the system is complete with the counting and result has settled to the correct number. It can be seen that it takes more clock cycles for the operation to complete (seen by the temporary result values and delay before the done signals) as there are increasingly more 1's to evaluate before the remaining values of A are 0, thus completing the operation. In Figure 1.5, very similar results appear as in Figure 1.4, the only difference being that each operation takes an equivalent amount of time since the operation cannot complete until the remaining bits of input A equal 0; since all of their leftmost bit (besides 8'b0) are 1, the operations all take the same amount of time. As an extra note, the testbench checks incrementing and decrementing the number of 1's in input A, therefore allowing for an easy to test and read waveform.

After the bitCounter module was thoroughly tested and proved to function as accordingly to the provided ASMD chart, a top level module DE1\_SoC\_task1.sv was created to implement the functionality on the FPGA board. The top level module instantiated the bitCounter.sv module with the inputs and outputs

corresponding to the DE1\_SoC board according to the specification described in the Task 1 procedure of this lab report. Submodule seg7.sv (created and tested in Lab 2) was utilized to display the results of the bit-counting system on hex-display HEX0. A testbench, DE1\_SoC\_task1\_tb, was then created. The testbench implemented the exact same tests as bitCounter\_tb by assigning the DE1\_SoC components/variable values equal to their corresponding bitCounter.sv variables; doing so allowed the same ‘initial begin’ code to be used for the DE1\_SoC. The waveform can be seen in the figure below:

 


Figure 1.7: DE1\_SoC\_task1 Waveform

The exact same tests as the bitCounter testbench were implemented and shown in the waveform; all explanations and testing performed on bitCounter\_tb apply here. CLOCK\_50 can be seen as the driving clock behind all modules, HEX0 displays the resulting total number of ON signals of input A, which itself is given its value by SW[7:0]. In other words, we can say that HEX0 should display the total count of how many switches are flipped on at the time when the start signal (KEY[9]) was turned on. When the operation is complete, LEDR[9] turns on, acting as the done signal. It is important to note that seg7.sv was used to convert 7-bit binary to the HEX display as created and tested in Lab 2. The waveform generated clearly depicts the expected results, as ‘result’ when ‘done’ is true is equal to the total number of switches (representing input A) are on at the time of when the start signal (KEY[9]) was switched on. All test cases passed and matched the same tested and verified waveforms and outputs of bitCounter\_tb; again, all explanations and testing of bitCounter\_tb apply here.

After verifying the DE1\_SoC bit-counting functionality, a demonstration video was recorded (found on Canvas), and a block diagram was created as found below:

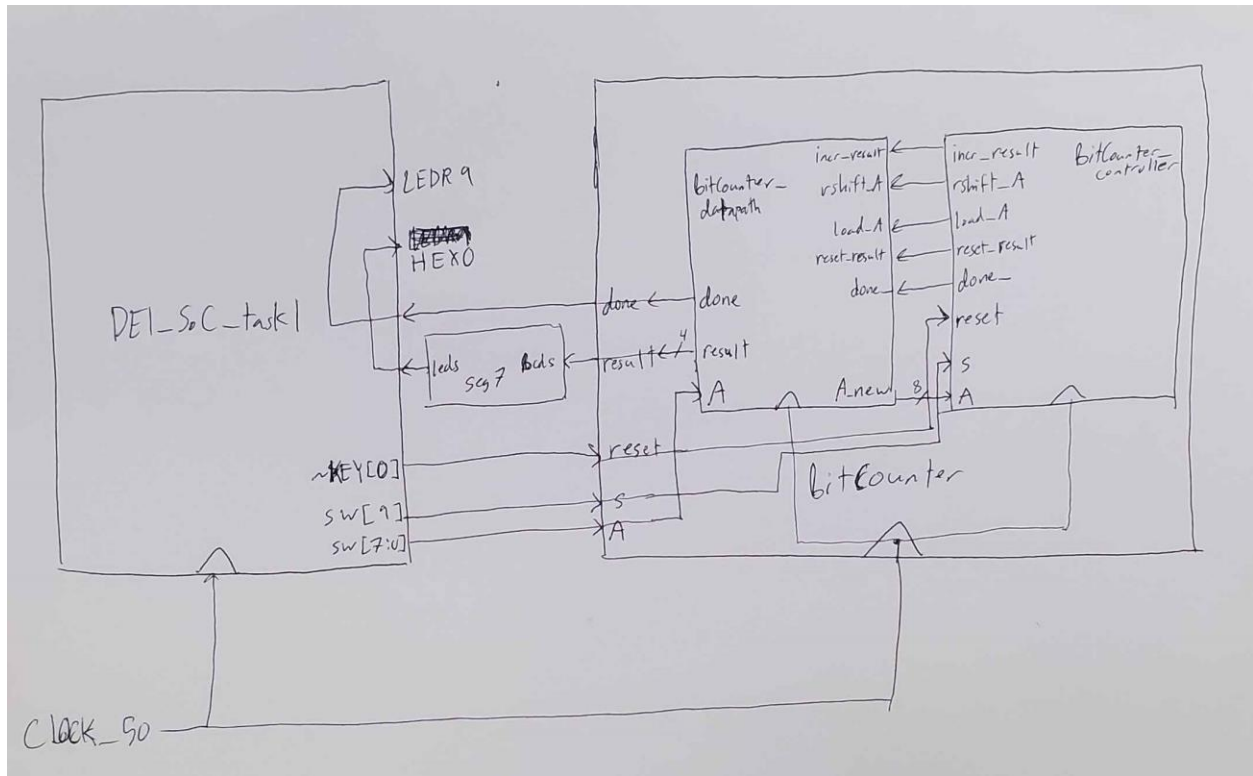


Figure 1.8: DE1\_SoC\_task1 Block Diagram

## Task 2: Binary Search Algorithm

Like task 1, task 2 was implemented by having a top-level module task2.sv, with submodules for the datapath and control modules. The datapath module controls the RAM where the values inside the binary search array are, and the control module is responsible for the FSM changing of states and the bounds where the binary search should look at during any point in the algorithm. This implementation has five-states: one idle, for waiting for a start signal; one state to run the algorithm and fetch a value at the address in between the bounds; one state to determine if the search has finished running; one state to adjust the bounds of the search before running the search again; and one state to stay at when the search has finished running. The algorithm generally works by fetching the value at the centermost address (initially, this will always be 15 since the address width of the RAM is 32) between two bounds (at addresses 0 and 32 initially) and check if the fetched value is the desired value being searched for. If it is not found, the value fetched will be compared to the desired value, and depending on if the fetched value is higher or lower than the desired, the bounds will be updated accordingly. This process repeats until the value is found, or the algorithm can no longer be run because the bounds are too small – meaning that the value was not found in the given array.

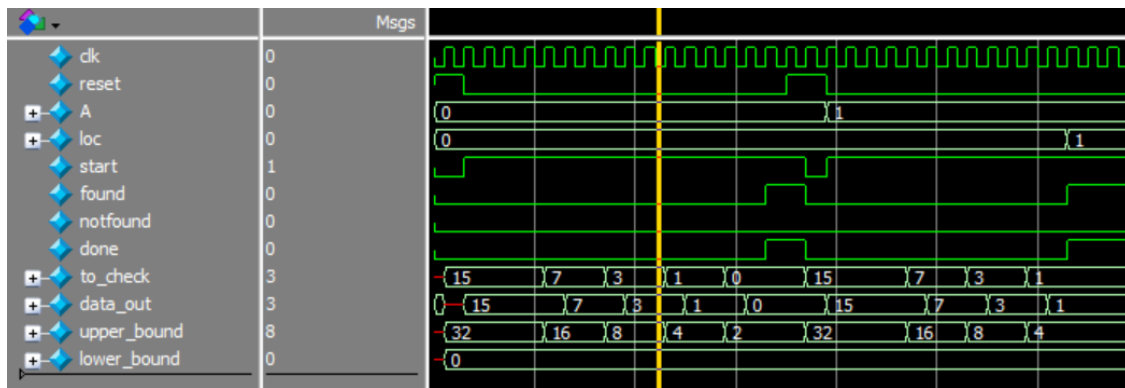


Figure 2.1: task2.sv Waveform, part 1

The testbench for the high-level module tested searching for the lowest value as an edge case, and the second lowest value as one of the values that takes the longest to get to. The upper bound changes to half the width of the current search size, and lower bound values do not range at all, as expected. At the end, when the value is found, the found and done values tick to high to indicate that the algorithm has finished running, and that the given value at A was found.

 


Figure 2.2: task2.sv Waveform, part 2

Next, the testbench tested for the highest and second highest values, for similar reasons as the tests above. For testing the value at array address 31, the notfound signal does tick up for a single clock cycle, but corrects itself quickly and shows the found signal alongside the done signal to indicate that the algorithm has fully and truly found the value and is confident in its result – meaning that the tiny uptick in notfound can be ignored. The address location loc also does not update until the algorithm finishes fully running. This issue is due to the way the edge case for the search of the last element in the array is handled – the bounds are adjusted when looking for values above 30 and creates a minor timing and compatibility issue when paired with the notfound logic. Looking for the value at address 30 works as normal.


 



Figure 2.3: task2.sv Waveform, part 3

Finally, the testbench tests what happens when the value at 16 is searched for, since 16 takes the maximum number of iterations to search for and has a combination of up and down binary search iterations. When the value at 15 is searched for, the value is found instantly, as expected. When a value that does not exist in the array, the notfound signal ticks up when the done signal goes high, as expected since the value could not be found.

 



 When tested with the DE1\_SoC in mind, the results mirror those of the original tests of task2.sv. The LEDRs linked up to the found, notfound, done, and reset signals all light up during correct situations as expected.



The testbenches for the control module described the behavior when the value returned from the address to\_check is not the desired value A, and when the value is in fact the desired value A. When it is not, the to\_check halves itself while the value is not found, indicating that the bounds are shifting correctly. When the value is found, the signal found and done goes to high, meaning the module detects the RAM array having the desired value.

Since the majority of the datapath module consists of the ram32x8 file to store values, only a brief iteration of all the values inside the RAM and confirmation was needed to ensure that the datapath was working.

After verifying the DE1\_SoC binary search functionality, a demonstration video was recorded (found on Canvas), and a block diagram was created as found below:



 


Figure 2.7: Full high-level block diagram for Task 2

### Final Product:

Overall, this lab provided a great opportunity to practice utilizing ASMD charts within the hardware-designing workflow, as well as a strong opportunity to practice and understand how datapath and controller components are different and how they work together to create a system's complete functionality. Task 1 allowed us to gain experience in implementing a hardware design *given* a specified ASMD chart; it was a completely new experience to have to analyze a very specific implementation and divide and implement it into its datapath and controller components. Task 2 helped develop the skills of drawing ASMD charts before implementing a project and streamlined the process for designing in SystemVerilog.

## Appendix: SystemVerilog Code

### 1) DE1\_SoC\_task1.sv

Date: November 13, 2024

DE1\_SoC\_task1.sv

Project: DE1\_SoC

```
1 //Aidan Lee, Aarin Wen
2 // 11/13/2024
3 // EE 371
4 // Lab 4
5
6 // Top level module to simulate bitCounter on the DE1_SoC board
7
8 // inputs:
9 // CLOCK_50          -> clk (clock signal for bitCounter)
10 // SW[7:0]           -> A   (input data for bitCounter)
11 // ~KEY[0] (pressing KEY[0]) -> reset (reset signal for bitCounter)
12
13 // outputs:
14 // LEDR[9] <- done   (bitCounter status signal; counting complete)
15 // HEX[0] <- results (bitCounter output; total 1's count of input A)
16
17 module DE1_SoC_task1 (
18     input logic [3:0] KEY,
19     input logic [9:0] SW,
20     input logic CLOCK_50,
21     output logic [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5,
22     output logic [9:0] LEDR);
23
24     // turn off unused HEX displays
25     assign HEX1 = 7'b1111111;
26     assign HEX2 = 7'b1111111;
27     assign HEX3 = 7'b1111111;
28     assign HEX4 = 7'b1111111;
29     assign HEX5 = 7'b1111111;
30
31     // logic variable to store result
32     logic [3:0] result;
33
34     // parameters, 8-bit wide A, 4 bits to store results
35     parameter A_WIDTH = 8;
36     parameter RES_WIDTH = 4;
37
38     // bitCounter instantiated with...
39     // parameters #(A_WIDTH, RES_WIDTH)
40     // clk      <- CLOCK_50
41     // A        <- SW[7:0]
42     // reset    <- ~KEY[0] (pressing KEY[0])
43     // done     -> LEDR[9]
44     // result   -> result (will display on HEX0 using seg7.sv)
45     bitCounter #(A_WIDTH, RES_WIDTH) bitCounter_
46     (.reset(~KEY[0]), .clk(CLOCK_50), .s(SW[9]), .A(SW[7:0]), .done(LEDR[9]), .result);
47
48     // display result on 7-segment display HEX0
49     // seg7 instantiated with results as input, HEX0 as output
50     seg7 HEX0_result (.bcd(result), .leds(HEX0));
51 endmodule
52
53 // DE1_SoC_task1.sv testbench; runs same test cases as bitCounter.sv
54 // tests reset and s cases as well as A <= 8'b10101010, 8'b10000001, and 8'b0;
55 module DE1_SoC_task1_tb ();
56     logic [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5;
57     logic [9:0] LEDR;
58     logic [3:0] KEY;
59     logic [9:0] SW;
60     logic CLOCK_50;
61
62     // instantiate DE1_SoC_task1 dut
63     DE1_SoC_task1 dut (.*);
64
65     // assign DE1_SoC variables to bitCounter counterparts
66     logic clk, s, reset;
67     logic [7:0] A;
68     assign CLOCK_50 = clk;
69     assign SW[7:0] = A;
70     assign SW[9] = s;
71     assign KEY[0] = ~reset;
72
73     // initialize clock simulation
```

```
74     parameter CLOCK_PERIOD = 100;
75     initial begin
76         clk <= 0;
77         forever #(CLOCK_PERIOD/2) clk <= ~clk;
78     end
79
80     // begin tests
81     integer i; // int i for loops
82     // begin tests
83     initial begin
84         // initialize values
85         reset <= 1; s <= 0; A <= 8'b0; @(posedge clk);
86
87         // release reset
88         reset <= 0; @(posedge clk);
89
90         // test if bit-count analysis begins without start signal (SHOULD NOT)
91         // results & done should remain at 0
92         A <= 8'b10101010; repeat (14) @(posedge clk);
93         A <= 8'b00000000; @(posedge clk);
94
95         // loop that uses bitCounter on bits 8'b00000001 to 8'b11111111 by incrementing
96         // results should settle to how many 1's are in the 8b input; expect 1->8
97         // done should have value '1' whenever results are settled
98         // note: 8b'0 will be checked in next loop
99         for (i = 0; i < 8; i = i + 1) begin
100             // turn start signal off before loading in new data
101             s <= 0; @(posedge clk);
102
103             // load in new A value
104             A <= (8'b00000001 << i) | A; @(posedge clk);
105
106             // count 1's and let 'result' and 'done' settle
107             s <= 1; repeat (14) @(posedge clk);
108         end
109
110         // loop that uses left shifting to bit-count 8'b11111111 to 8'b0
111         // results should settle to how many 1's are in the 8b input; expect 8->0
112         // done should have value '1' whenever results are settled
113         for (i = 8; i >= 0; i = i - 1) begin
114             // turn start signal off before loading in new data
115             s <= 0; @(posedge clk);
116
117             // load in new A value
118             A <= 8'b11111111 << (8-i); @(posedge clk);
119
120             // count 1's and let 'result' and 'done' settle
121             s <= 1; repeat (14) @(posedge clk);
122         end
123     $stop;
124 end
125 endmodule
126
```

## 2) bitCounter.sv

Date: November 13, 2024

bitCounter.sv

Project: DE1\_SoC

```
1  //Aidan Lee, Aarin Wen
2  // 11/13/2024
3  // EE 371
4  // Lab 4
5
6  // Main bitCounter module
7  // Counts the number of 1's in input A and outputs total as 'result' and a 'done' signal
8
9  // Parameters: A_WIDTH (width of input A) and RES_WIDTH (width of result)
10
11 // inputs:
12 // 1'b wide: reset, clk, s (start signal),
13 // A_WIDTH wide: A (data input)
14
15 // outputs:
16 // 1'b wide: done (counting complete)
17 // RES_WIDTH wide: result (total count of 1's in A)
18
19 module bitCounter #(parameter A_WIDTH = 8, RES_WIDTH = 4) (
20     input logic reset, clk, s,
21     input logic [A_WIDTH-1:0] A,
22     output logic done,
23     output logic [RES_WIDTH-1:0] result);
24
25     // logic for control signals and updated A value
26     logic incr_result, rshift_A, load_A, reset_result, done_;
27     logic [A_WIDTH-1:0] A_new;
28
29     // initialize datapath
30     // all inputs and outputs instantiated with their respective matching variables
31     bitCounter_datapath #(A_WIDTH, RES_WIDTH) datapath
32     (.clk, .incr_result, .rshift_A, .load_A, .reset_result, .done_, .A, .done, .A_new, .
33     result);
34
35     // initialize controller
36     // all inputs and outputs besides A instantiated with their respective matching variables
37     // input 'A' is instantiated with 'A_new' which is the updated A value from the datapath
38     bitCounter_controller #(A_WIDTH, RES_WIDTH) controller
39     (.reset, .clk, .s, .A(A_new), .incr_result, .rshift_A, .load_A, .reset_result, .done_);
40
41 endmodule
42
43 ///////////////////////////////////////////////////////////////////
44 // bitCounter datapath module
45 // Contains all datapath elements and data operations of bitCounter,
46 // also outputs updated A value for controller
47
48 // Parameters: A_WIDTH (width of input A) and RES_WIDTH (width of result)
49
50 // inputs:
51 // 1'b wide: clk,
52 // incr_result, rshift_a, load_A, reset_result, done_ (signals from controller)
53 // A_WIDTH wide: A (input data)
54
55 // outputs:
56 // 1'b wide: done (count complete status signal)
57 // A_WIDTH wide: A_new (updated A value for controller)
58 // RES_WIDTH wide: result (total 1's in A)
59
60 module bitCounter_datapath #(parameter A_WIDTH = 8, RES_WIDTH = 4) (
61     input logic clk, incr_result, rshift_A, load_A, reset_result, done_,
62     input logic [A_WIDTH-1:0] A,
63     output logic done,
64     output logic [A_WIDTH-1:0] A_new,
65     output logic [RES_WIDTH-1:0] result);
66
67     // always_ff block to synchronously manipulate and move data
68     always_ff @(posedge clk) begin
69         done <= done_; // store 'done'
70
71         if (incr_result) // increment result
72             result <= result + 1'b1;
```

```

73
74     if (rshift_A) // right shift A by 1
75         A_new <= A_new >> 1'b1;
76
77     if (load_A) // load A
78         A_new <= A;
79
80     if (reset_result) // set result = 0
81         result <= 0;
82 end
83
84 endmodule
85
86 ///////////////////////////////////////////////////////////////////
87
88 // bitCounter controller module
89 // Contains all controller elements of bitCounter including FSM,
90 // also takes in and utilizes updated A value from datapath output
91 // also contains logic and operations to output correct control signals
92
93 // Parameters: A_WIDTH (width of input A) and RES_WIDTH (width of result)
94
95 // inputs:
96 // 1'b wide: reset, clk, s (start signal)
97 // A_WIDTH wide: A (input data)
98
99 // outputs:
100 // 1'b wide: incr_result, (increment results)
101 //           rshift_A, (right shift A by 1 bit)
102 //           load_A, (load new A value)
103 //           reset_result, (reset result value to 0)
104 //           done_ (count complete signal)
105
106 module bitCounter_controller #(parameter A_WIDTH = 8, RES_WIDTH = 4) (
107     input logic reset, clk, s,
108     input logic [A_WIDTH-1:0] A,
109     output logic incr_result, rshift_A, load_A, reset_result, done_);
110
111     // present and next states S1 S2 S3
112     enum {S1, S2, S3} ps, ns; // S1 = initialization, S2 = analyzing, S3 = finished
113
114     // FSM state-to-state logic
115     always_comb begin
116         case (ps)
117             S1: ns = s ? S2: S1; // ns to S2 if s, S1 OW
118             S2: ns = (A == 0) ? S3: S2; // ns to S3 if A==0, S2 OW
119             S3: ns = s ? S3: S1; // ns to S3 if s, S1 OW
120         endcase
121     end
122
123     // combinational logic for output control signals
124     always_comb begin
125         // increment signal if in S2, A != 0 and rightmost bit == 1
126         incr_result = (ps == S2) & (ns == S2) & (A[0] == 1);
127         // right shift signal if ps is S2 (data analyzing and unfinished)
128         rshift_A = ps == S2;
129         // load signal if data analyzing hasnt started yet & no start signal
130         load_A = (ps == S1) & (~s);
131         // reset result signal if data analyzing for current data hasnt started
132         reset_result = ps == S1;
133         // send done signal if data analyzing is complete
134         done_ = ps == S3;
135     end
136
137     // ps <= ns unless reset, then ps resets to S1
138     always_ff @(posedge clk) begin
139         if (reset)
140             ps <= S1;
141         else
142             ps <= ns;
143     end
144 end
145

```

```

146 endmodule
147
148 ///TESTBENCHES////////////////////////////////////
149
150 // main testbench
151 // tests reset and s cases as well as A <= 8'b10101010, 8'b10000001, and 8'b0;
152 module bitCounter_tb();
153 // variables and parameters
154 parameter A_WIDTH = 8;
155 parameter RES_WIDTH = 4;
156 logic reset, clk, s, done;
157 logic [A_WIDTH-1:0] A;
158 logic [RES_WIDTH-1:0] result;
159
160 // create bitCounter dut
161 bitCounter #(A_WIDTH, RES_WIDTH) dut (.*);
162
163 // initialize clock simulation
164 parameter CLOCK_PERIOD = 100;
165 initial begin
166     clk <= 0;
167     forever #(CLOCK_PERIOD/2) clk <= ~clk;
168 end
169
170 integer i; // int i for loops
171 // begin tests
172 initial begin
173     // initialize values
174     reset <= 1; s <= 0; A <= 8'b0; @(posedge clk);
175
176     // release reset
177     reset <= 0; @(posedge clk);
178
179     // test if bit-count analysis begins without start signal (SHOULD NOT)
180     // results & done should remain at 0
181     A <= 8'b10101010; repeat (14) @(posedge clk);
182     A <= 8'b00000000; @(posedge clk);
183
184     // loop that uses bitCounter on bits 8'b00000001 to 8'b11111111 by incrementing
185     // results should settle to how many 1's are in the 8b input; expect 1->8
186     // done should have value '1' whenever results are settled
187     // note: 8b'0 will be checked in next loop
188     for (i = 0; i < 8; i = i + 1) begin
189         // turn start signal off before loading in new data
190         s <= 0; @(posedge clk);
191
192         // load in new A value
193         A <= (8'b00000001 << i) | A; @(posedge clk);
194
195         // count 1's and let 'result' and 'done' settle
196         s <= 1; repeat (14) @(posedge clk);
197     end
198
199     // loop that uses left shifting to bit-count 8'b11111111 to 8'b0
200     // results should settle to how many 1's are in the 8b input; expect 8->0
201     // done should have value '1' whenever results are settled
202     for (i = 8; i >= 0; i = i - 1) begin
203         // turn start signal off before loading in new data
204         s <= 0; @(posedge clk);
205
206         // load in new A value
207         A <= 8'b11111111 << (8-i); @(posedge clk);
208
209         // count 1's and let 'result' and 'done' settle
210         s <= 1; repeat (14) @(posedge clk);
211     end
212     $stop;
213
214 end
215 endmodule
216
217 // datapath testbench
218 module bitCounter_datapath_tb();

```

```

219 // variables and parameters
220 parameter A_WIDTH = 8;
221 parameter RES_WIDTH = 4;
222 logic clk, incr_result, rshift_A, load_A, reset_result, done_;
223 logic [A_WIDTH-1:0] A;
224
225 logic done;
226 logic [A_WIDTH-1:0] A_new;
227 logic [RES_WIDTH-1:0] result;
228
229 // create bitCounter dut
230 bitCounter_datapath #(A_WIDTH, RES_WIDTH) dut2 (.*);
231
232 // initialize clock simulation
233 parameter CLOCK_PERIOD = 100;
234 initial begin
235     clk <= 0;
236     forever #(CLOCK_PERIOD/2) clk <= ~clk;
237 end
238
239 initial begin
240     // initialize values
241     incr_result <= 0;
242     rshift_A <= 0;
243     load_A <= 0;
244     reset_result <= 1;
245     done_ <= 0;
246
247     // test load_A, new data A = 8'b10101010 should load in.
248     A <= 8'b10101010;
249     load_A <= 1; @(posedge clk);
250     load_A <= 0; @(posedge clk);
251
252     // test incrementing, result should increment from decimal 0 to 8
253     reset_result <= 0;
254     incr_result <= 1; repeat (8) @(posedge clk);
255     incr_result <= 0; @(posedge clk);
256
257     // test reset_result, result should go to 0
258     reset_result <= 1; @(posedge clk);
259     reset_result <= 0; @(posedge clk);
260
261     // test right shift A, A_new should now equal 8'b01010101
262     rshift_A <= 1; @(posedge clk);
263     rshift_A <= 0; @(posedge clk);
264
265     // test loading in new value A
266     A <= 8'b11110000;
267     load_A <= 1; @(posedge clk);
268     load_A <= 0; @(posedge clk);
269
270     // test that done stores and outputs done_ (output from controller)
271     done_ <= 1; @(posedge clk);
272     done_ <= 0; @(posedge clk);
273
274     $stop;
275
276 end
277 endmodule
278
279 // Controller testbench
280 module bitCounter_controller_tb();
281 // parameters
282 parameter A_WIDTH = 8;
283 parameter RES_WIDTH = 4;
284
285 // signals for inputs and outputs
286 logic reset, clk, s;
287 logic [A_WIDTH-1:0] A;
288
289 logic incr_result, rshift_A, load_A, reset_result, done_;
290
291

```



```

292 // instantiate the controller
293 bitCounter_controller #(A_WIDTH, RES_WIDTH) dut3 (.*);
294
295 // initialize clock simulation
296 parameter CLOCK_PERIOD = 100;
297 initial begin
298     clk <= 0;
299     forever #(CLOCK_PERIOD/2) clk <= ~clk;
300 end
301
302 // test sequence
303 initial begin
304     // initialize inputs
305     reset <= 1;
306     s <= 0;
307     A <= 8'b0;
308     @(posedge clk);
309
310     // Release reset, enter S1
311     // Expect: reset_result = 1, all other signals = 0
312     reset <= 0; @(posedge clk);
313
314     // Test S1 to S2 transition with s = 1
315     s <= 1; A <= 8'b01010101; @(posedge clk);
316     // Expect: load_A = 1, all other signals = 0
317
318     // Test S2 state behavior with non-zero A (data analyzing)
319     s <= 0; repeat(2) @(posedge clk);
320     // Expect:
321     // rshift_A = 1
322     // incr_result = 1 since least significant bit of A is 1
323     // all other signals = 0
324
325     // Test S2 to S3 transition when A == 0
326     A <= 8'b0; @(posedge clk);
327     // Expect: done_ = 1 (indicates counting is complete), all other signals = 0
328
329     // Test S3 to S1 transition when s is toggled
330     s <= 1; @(posedge clk);
331     // Expect:
332     // done_ remains 1 if in S3, indicating analyzing is complete
333     // done_ returns to 0 upon resetting back to S1 given s = 0
334     s <= 0; @(posedge clk);
335
336     // test if loading in new value works
337     A <= 8'b11110000;
338     s <= 1; @(posedge clk);
339     s <= 0; repeat(2) @(posedge clk);
340
341     $stop;
342 end
343 endmodule
344
345

```

### 3) seg7.sv

Date: November 13, 2024

seg7.sv

Project: DE1\_SoC

```
1 // Aidan Lee, Aarin Wen
2 // 10/18/2024
3 // EE 371
4 // Lab 2
5
6 // Converts decimal number to 7-segment display in HEX
7 // input bcd represents decimal number up to 15 (4 bits)
8 // output leds represents binary output for 7-seg display (7 bits)
9
10 module seg7 (bcd, leds);
11     input logic [3:0] bcd;
12     output logic [6:0] leds;
13
14     // decimal to 7-seg block
15     always_comb begin
16         case (bcd)
17             // Light: 6543210
18             4'b0000: leds = 7'b1000000; // 0
19             4'b0001: leds = 7'b1111001; // 1
20             4'b0010: leds = 7'b0100100; // 2
21             4'b0011: leds = 7'b0110000; // 3
22             4'b0100: leds = 7'b0011001; // 4
23             4'b0101: leds = 7'b0010010; // 5
24             4'b0110: leds = 7'b0000010; // 6
25             4'b0111: leds = 7'b1111000; // 7
26             4'b1000: leds = 7'b0000000; // 8
27             4'b1001: leds = 7'b0010000; // 9
28             4'b1010: leds = 7'b0001000; // A
29             4'b1011: leds = 7'b0000011; // B
30             4'b1100: leds = 7'b1000110; // C
31             4'b1101: leds = 7'b0100001; // D
32             4'b1110: leds = 7'b0000110; // E
33             4'b1111: leds = 7'b0001110; // F
34             default: leds = 7'bx;
35         endcase
36     end
37 endmodule
38
39 // seg7 testbench:
40 module seg7_testbench();
41     logic [3:0] bcd;
42     logic [6:0] leds;
43
44     //dut instantiation
45     seg7 dut (bcd, leds);
46
47     int i;
48     initial begin
49         // increment inputs 0 to 15, expect outputs 0 to F
50         for (i = 0; i <= 15; i++) begin
51             bcd = i; #50;
52         end
53
54         // decrement inputs 15 to 0, expect outputs F to 0
55         for (i = 15; i >= 0; i--) begin
56             bcd = i; #50;
57         end
58
59         $stop;
60     end
61 endmodule
62
```

**4) De1\_SoC.sv (task 2)**

```

1 timescale 1ns/1ns
2
3 // Aidan Lee, Aarin Wen
4 // 11/13/2024
5 // EE 371
6 // Lab 4
7
8 // Binary search module that returns the address loc in Sw[7:0] sorted ascending 32x8 ram module if Sw[7:0] value Sw[7:0] is found.
9 // Searches the middle most value of the array. If not found, the module decides whether to search
10 // the upper or lower half depending on if the value found at the middle is higher or lower than the
11 // the desired value. Needs RAM to be sorted ascending to work.
12
13 // utilizes clk input
14 input reset          resets the search (clears the output) and waits for another Sw[9] signal
15 input [7:0] A         represents the value that you want to find inside the
16 input start          represents the y coordinates of the two endpoints of the line you want to draw
17 output found         goes high if the value Sw[7:0] was found in the ram
18 output final_notfound goes high if the value Sw[7:0] was not found
19 output done          goes high if algorithm is finished
20 output [4:0] loc     represents the address location where the value is found
21
22 module DelSoC (CLOCK_50, KEY, SW, HEX0, HEX1, HEX2, HEX3, HEX4, HEX5, LEDR);
23
24 input logic CLOCK_50;
25 input logic [3:0] KEY;
26 input logic [9:0] SW;
27 output logic [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5;
28 output logic [9:0] LEDR;
29
30 logic clk, reset, done, found, notfound;
31 logic [4:0] loc;
32 logic [7:0] result;
33
34 logic start;
35
36 assign reset = ~KEY[0]; // reset on KEY0
37 assign start = SW[9]; // start on SW9
38 assign LEDR[9] = found; // 9 lights up if found
39 assign LEDR[8] = notfound; // 8 lights up if not found
40 assign LEDR[1] = done; // 1 indicates finished
41 assign LEDR[0] = reset; // 0 indicates currently in reset
42
43 assign clk = CLOCK_50;
44
45 // main binary search algorithm
46 // takes in clock and reset
47 // takes in Sw[7:0] as the value to look for in binary search
48 // takes in Sw[9] to indicate that the algorithm should Sw[9] running
49 // gives out found and notfound depending on if the value was found in ram
50 // gives out done when finished looking for value
51 // gives out loc which is the address where the desired value Sw[7:0] is stored
52 task2 taskDisp2 (reset, clk, SW[7:0], start, found, notfound, done, loc); // SW[7:0] to specify A
53 seg7 disp1 ({1'b0, loc[4:0]}, HEX1);
54 seg7 disp0 (loc[3:0], HEX0);
55
56 // none of the other hexes are used for this task
57
58 assign HEX2 = 7'b1111111;
59 assign HEX3 = 7'b1111111;
60 assign HEX4 = 7'b1111111;
61 assign HEX5 = 7'b1111111;
62
63 // kill all other leds
64 assign LEDR[7:2] = 6'b000000;
65
66 endmodule
67
68 module DelSoC_tb ();
69 logic CLOCK_50;
70 logic [3:0] KEY;
71 logic [9:0] SW;
72 logic [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5;
73 logic [9:0] LEDR;
74
75 logic clk;
76 assign CLOCK_50 = clk;
77
78 // Clock logic
79 parameter CLOCK_PERIOD = 5; // Increase clock frequency
80 initial begin
81     clk <= 0;
82     forever #(CLOCK_PERIOD/2) clk <= ~clk; // Forever toggle the clock
83 end
84
85 DelSoC dut (. *);
86
87 initial begin
88     SW[7:0] <= 8'b00000000; SW[9] <= 1'b0;
89     KEY[0] <= 0; @(posedge clk);
90     @(posedge clk);
91
92     // test very end
93     SW[9] <= 1'b1; KEY[0] <= 1; SW[7:0] <= 8'b00000000;
94     repeat (16) @(posedge clk);
95
96     KEY[0] <= 0; @(posedge clk); // check if reset works
97     SW[9] <= 1'b0; @(posedge clk);
98
99     // test lowest value of binary search that takes the longest time
100     SW[9] <= 1'b1; KEY[0] <= 1; SW[7:0] <= 8'b00000001;
101     repeat (16) @(posedge clk);
102
103     SW[9] <= 1'b0;
104     KEY[0] <= 0; @(posedge clk);
105     @(posedge clk);
106
107     // test highest value (edge case)
108     SW[9] <= 1'b1; KEY[0] <= 1; SW[7:0] <= 8'd31;
109     repeat (24) @(posedge clk);
110
111     SW[9] <= 1'b0;
112     KEY[0] <= 0; @(posedge clk);
113     @(posedge clk);
114

```

```

115
116 // test highest value of binary search that takes the longest time
117 SW[9] <= 1'b1; KEY[0] <= 1; SW[7:0] <= 8'd30;
118 repeat (16) @(posedge clk);
119
120 SW[9] <= 1'b0;
121 KEY[0] <= 0; @(posedge clk);
122     @(posedge clk);
123
124 // test SW[7:0] value of binary search in the middle that takes the longest time
125 // to test that going up and down works
126 SW[9] <= 1'b1; KEY[0] <= 1; SW[7:0] <= 8'd16;
127 repeat (16) @(posedge clk);
128
129 SW[9] <= 1'b0;
130 KEY[0] <= 0; @(posedge clk);
131     @(posedge clk);
132
133 // test finding the value immediately
134 SW[9] <= 1'b1; KEY[0] <= 1; SW[7:0] <= 8'd15;
135 repeat (16) @(posedge clk);
136
137 SW[9] <= 1'b0;
138 KEY[0] <= 0; @(posedge clk);
139     @(posedge clk);
140
141 // test value not in array
142 SW[9] <= 1'b1; KEY[0] <= 1; SW[7:0] <= 8'b11111111;
143 repeat (24) @(posedge clk);
144 SW[9] <= 1'b0; @(posedge clk); @(posedge clk);
145
146 $stop;
147 end
148
149 endmodule

```

5) **task2.sv**

```

1 timescale 1ns/1ns
2
3 // Aidan Lee, Aarin Wen
4 // 11/13/2024
5 // EE 371
6 // Lab 4
7 //
8 // Binary search module that returns the address loc in a sorted ascending 32x8 ram module if a value A is found.
9 // Searches the middle most value of the array. If not found, the module decides whether to search
10 // the upper or lower half depending on if the value found at the middle is higher or lower than the
11 // the desired value. Needs RAM to be sorted ascending to work.
12 //
13 // utilizes clk input
14 // input reset resets the search (clears the output) and waits for another start signal
15 // input [7:0] A represents the value that you want to find inside the
16 // input start represents the y coordinates of the two endpoints of the line you want to draw
17 // output found goes high if the value A was found in the ram
18 // output notfound goes high at the end when finished if the value A was not found
19 // output done goes high if algorithm is finished
20 // output [4:0] loc represents the address location where the value is found
21
22 module task2 (reset, clk, A, start, found, notfound, done, loc);
23
24     input logic reset, clk, start;
25     input logic [7:0] A;
26
27     output logic found, notfound, done;
28     output logic [4:0] loc;
29
30     // intermediate values to talk between datapath and control
31     logic [4:0] to_check;
32     logic [7:0] data_out;
33
34     task2_datapath d_unit (.*);
35     task2_control c_unit (.*);
36
37 endmodule
38
39 module task2_tb ();
40     logic reset, clk;
41     logic [7:0] A;
42     logic [4:0] loc;
43     logic start, found, notfound, done;
44
45     // clock logic
46     parameter CLOCK_PERIOD = 5; // Increase clock frequency
47     initial begin
48         clk = 0;
49         forever # (CLOCK_PERIOD/2) clk = ~clk; // Forever toggle the clock
50     end
51
52     task2 dut (.*);
53
54     initial begin
55         A <= 8'b00000000; start <= 1'b0;
56         reset <= 1; @(posedge clk);
57         @(posedge clk);
58
59         // test very end
60         start <= 1'b1; reset <= 0; A <= 8'b00000000;
61         repeat (16) @(posedge clk);
62
63         reset <= 1; @(posedge clk); // check if reset works
64         start <= 1'b0; @(posedge clk);
65
66         // test lowest value of binary search that takes the longest time
67         start <= 1'b1; reset <= 0; A <= 8'b00000001;
68         repeat (16) @(posedge clk);
69
70         start <= 1'b0;
71         reset <= 1; @(posedge clk);
72         start <= 1'b0;
73         reset <= 1; @(posedge clk);
74         start <= 1'b0;
75         reset <= 1; @(posedge clk);
76
77         // test highest value (edge case)
78         start <= 1'b1; reset <= 0; A <= 8'd31;
79         repeat (24) @(posedge clk);
80
81         start <= 1'b0;
82         reset <= 1; @(posedge clk);
83         start <= 1'b0;
84         reset <= 1; @(posedge clk);
85
86         // test highest value of binary search that takes the longest time
87         start <= 1'b1; reset <= 0; A <= 8'd30;
88         repeat (16) @(posedge clk);
89
90         start <= 1'b0;
91         reset <= 1; @(posedge clk);
92         start <= 1'b0;
93         reset <= 1; @(posedge clk);
94
95         // test a value of binary search in the middle that takes the longest time
96         // to test that going up and down works
97         start <= 1'b1; reset <= 0; A <= 8'd16;
98         repeat (16) @(posedge clk);
99
100         start <= 1'b0;
101         reset <= 1; @(posedge clk);
102         start <= 1'b0;
103         reset <= 1; @(posedge clk);
104
105         // test finding the value immediately
106         start <= 1'b1; reset <= 0; A <= 8'd15;
107         repeat (16) @(posedge clk);
108
109         start <= 1'b0;
110         reset <= 1; @(posedge clk);
111         start <= 1'b1; reset <= 0; A <= 8'b11111111;
112         repeat (24) @(posedge clk);
113         start <= 1'b0; @(posedge clk); @(posedge clk);
114
115         $stop;

```



```
115 | end  
116 |  
117 endmodule
```

## 6) my\_array.mif

```
-- Copyright (C) 2017 Intel Corporation. All rights reserved.
-- Your use of Intel Corporation's design tools, logic functions
-- and other software and tools, and its AMPP partner logic
-- functions, and any output files from any of the foregoing
-- (including device programming or simulation files), and any
-- associated documentation or information are expressly subject
-- to the terms and conditions of the Intel Program License
-- Subscription Agreement, the Intel Quartus Prime License Agreement,
-- the Intel MegaCore Function License Agreement, or other
-- applicable license agreement, including, without limitation,
-- that your use is for the sole purpose of programming logic
-- devices manufactured by Intel and sold by Intel or its
-- authorized distributors. Please refer to the applicable
-- agreement for further details.

-- Quartus Prime generated Memory Initialization File (.mif)

WIDTH=8;
DEPTH=32;

ADDRESS_RADIX=UNS;
DATA_RADIX=UNS;

CONTENT BEGIN
    0   : 0;
    1   : 1;
    2   : 2;
    3   : 3;
    4   : 4;
    5   : 5;
    6   : 6;
    7   : 7;
    8   : 8;
    9   : 9;
    10  : 10;
    11  : 11;
    12  : 12;
    13  : 13;
    14  : 14;
    15  : 15;
    16  : 16;
    17  : 17;
    18  : 18;
    19  : 19;
    20  : 20;
    21  : 21;
    22  : 22;
    23  : 23;
    24  : 24;
    25  : 25;
    26  : 26;
    27  : 27;
    28  : 28;
    29  : 29;
    30  : 30;
    31  : 31;

END;
```

## 7) ram32x8.v

Date: November 13, 2024

ram32x8.v

Project: DE1\_SoC

```
1  // megafunction wizard: %RAM: 1-PORT%
2  // GENERATION: STANDARD
3  // VERSION: WM1.0
4  // MODULE: altsyncram
5
6  // =====
7  // File Name: ram32x8.v
8  // Megafunction Name(s):
9  //     altsyncram
10 //
11 // Simulation Library Files(s):
12 //     altera_mf
13 // =====
14 // *****
15 // THIS IS A WIZARD-GENERATED FILE. DO NOT EDIT THIS FILE!
16 //
17 // 17.0.0 Build 595 04/25/2017 SJ Lite Edition
18 // *****
19
20
21 //Copyright (C) 2017 Intel Corporation. All rights reserved.
22 //Your use of Intel Corporation's design tools, logic functions
23 //and other software and tools, and its AMPP partner logic
24 //functions, and any output files from any of the foregoing
25 //(including device programming or simulation files), and any
26 //associated documentation or information are expressly subject
27 //to the terms and conditions of the Intel Program License
28 //Subscription Agreement, the Intel Quartus Prime License Agreement,
29 //the Intel MegaCore Function License Agreement, or other
30 //applicable license agreement, including, without limitation,
31 //that your use is for the sole purpose of programming logic
32 //devices manufactured by Intel and sold by Intel or its
33 //authorized distributors. Please refer to the applicable
34 //agreement for further details.
35
36
37 // synopsys translate_off
38 timescale 1 ps / 1 ps
39 // synopsys translate_on
40 module ram32x8 (
41     address,
42     clock,
43     data,
44     wren,
45     q);
46
47     input [4:0] address;
48     input clock;
49     input [7:0] data;
50     input wren;
51     output [7:0] q;
52 `ifndef ALTERA_RESERVED_QIS
53 // synopsys translate_off
54     tri1 clock;
55 `ifndef ALTERA_RESERVED_QIS
56 // synopsys translate_on
57     endif
58
59     wire [7:0] sub_wire0;
60     wire [7:0] q = sub_wire0[7:0];
61
62     altsyncram altsyncram_component (
63         .address_a (address),
64         .clock0 (clock),
65         .data_a (data),
66         .wren_a (wren),
67         .q_a (sub_wire0),
68         .aclr0 (1'b0),
69         .aclr1 (1'b0),
70         .address_b (1'b1),
71         .addressstall_a (1'b0),
72         .addressstall_b (1'b0),
73
```

```

74         .byteena_a (1'b1),
75         .byteena_b (1'b1),
76         .clock1 (1'b1),
77         .clocken0 (1'b1),
78         .clocken1 (1'b1),
79         .clocken2 (1'b1),
80         .clocken3 (1'b1),
81         .data_b (1'b1),
82         .eccstatus (),
83         .q_b (),
84         .rden_a (1'b1),
85         .rden_b (1'b1),
86         .wren_b (1'b0));
87
88     defparam
89         altsyncram_component.clock_enable_input_a = "BYPASS",
90         altsyncram_component.clock_enable_output_a = "BYPASS",
91         altsyncram_component.init_file = "my_array.mif",
92         altsyncram_component.intended_device_family = "Cyclone V",
93         altsyncram_component.lpm_hint = "ENABLE_RUNTIME_MOD=NO",
94         altsyncram_component.lpm_type = "altsyncram",
95         altsyncram_component.numwords_a = 32,
96         altsyncram_component.operation_mode = "SINGLE_PORT",
97         altsyncram_component.outdata_aclr_a = "NONE",
98         altsyncram_component.outdata_reg_a = "UNREGISTERED",
99         altsyncram_component.power_up_uninitialized = "FALSE",
100        altsyncram_component.ram_block_type = "M10K",
101        altsyncram_component.read_during_write_mode_port_a = "NEW_DATA_NO_NBE_READ",
102        altsyncram_component.width_a = 5,
103        altsyncram_component.width_a = 8,
104        altsyncram_component.width_byteena_a = 1;
105
106    endmodule
107
108    // =====
109    // CNX file retrieval info
110    // =====
111    // Retrieval info: PRIVATE: ADDRESSSTALL_A NUMERIC "0"
112    // Retrieval info: PRIVATE: Ac1rAddr NUMERIC "0"
113    // Retrieval info: PRIVATE: Ac1rByte NUMERIC "0"
114    // Retrieval info: PRIVATE: Ac1rData NUMERIC "0"
115    // Retrieval info: PRIVATE: Ac1rOutput NUMERIC "0"
116    // Retrieval info: PRIVATE: BYTE_ENABLE NUMERIC "0"
117    // Retrieval info: PRIVATE: BYTE_SIZE NUMERIC "8"
118    // Retrieval info: PRIVATE: BlankMemory NUMERIC "0"
119    // Retrieval info: PRIVATE: CLOCK_ENABLE_INPUT_A NUMERIC "0"
120    // Retrieval info: PRIVATE: CLOCK_ENABLE_OUTPUT_A NUMERIC "0"
121    // Retrieval info: PRIVATE: Clken NUMERIC "0"
122    // Retrieval info: PRIVATE: DataBusSeparated NUMERIC "1"
123    // Retrieval info: PRIVATE: IMPLEMENT_IN_LES NUMERIC "0"
124    // Retrieval info: PRIVATE: INIT_FILE_LAYOUT STRING "PORT_A"
125    // Retrieval info: PRIVATE: INIT_TO_SIM_X NUMERIC "0"
126    // Retrieval info: PRIVATE: INTENDED_DEVICE_FAMILY STRING "Cyclone V"
127    // Retrieval info: PRIVATE: JTAG_ENABLED NUMERIC "0"
128    // Retrieval info: PRIVATE: JTAG_ID STRING "NONE"
129    // Retrieval info: PRIVATE: MAXIMUM_DEPTH NUMERIC "0"
130    // Retrieval info: PRIVATE: MIFfilename STRING "ram32x8.mif"
131    // Retrieval info: PRIVATE: NUMWORDS_A NUMERIC "32"
132    // Retrieval info: PRIVATE: RAM_BLOCK_TYPE NUMERIC "2"
133    // Retrieval info: PRIVATE: READ_DURING_WRITE_MODE_PORT_A NUMERIC "3"
134    // Retrieval info: PRIVATE: RegAddr NUMERIC "1"
135    // Retrieval info: PRIVATE: RegData NUMERIC "1"
136    // Retrieval info: PRIVATE: RegOutput NUMERIC "0"
137    // Retrieval info: PRIVATE: SYNTH_WRAPPER_GEN_POSTFIX STRING "0"
138    // Retrieval info: PRIVATE: SingleClock NUMERIC "1"
139    // Retrieval info: PRIVATE: UseDQRAM NUMERIC "1"
140    // Retrieval info: PRIVATE: WRCONTROL_ACLR_A NUMERIC "0"
141    // Retrieval info: PRIVATE: WidthAddr NUMERIC "5"
142    // Retrieval info: PRIVATE: WidthData NUMERIC "8"
143    // Retrieval info: PRIVATE: rden NUMERIC "0"
144    // Retrieval info: LIBRARY: altera_mf altera_mf.components.all
145    // Retrieval info: CONSTANT: CLOCK_ENABLE_INPUT_A STRING "BYPASS"
146    // Retrieval info: CONSTANT: CLOCK_ENABLE_OUTPUT_A STRING "BYPASS"

```

```

147 // Retrieval info: CONSTANT: INIT_FILE STRING "ram32x8.mif"
148 // Retrieval info: CONSTANT: INTENDED_DEVICE_FAMILY STRING "Cyclone V"
149 // Retrieval info: CONSTANT: LPM_HINT STRING "ENABLE_RUNTIME_MOD=NO"
150 // Retrieval info: CONSTANT: LPM_TYPE STRING "altsyncram"
151 // Retrieval info: CONSTANT: NUMWORDS_A NUMERIC "32"
152 // Retrieval info: CONSTANT: OPERATION_MODE STRING "SINGLE_PORT"
153 // Retrieval info: CONSTANT: OUTDATA_ACLR_A STRING "NONE"
154 // Retrieval info: CONSTANT: OUTDATA_REG_A STRING "UNREGISTERED"
155 // Retrieval info: CONSTANT: POWER_UP_UNINITIALIZED STRING "FALSE"
156 // Retrieval info: CONSTANT: RAM_BLOCK_TYPE STRING "M10K"
157 // Retrieval info: CONSTANT: READ_DURING_WRITE_MODE_PORT_A STRING "NEW_DATA_NO_NBE_READ"
158 // Retrieval info: CONSTANT: WIDTHAD_A NUMERIC "5"
159 // Retrieval info: CONSTANT: WIDTH_A NUMERIC "8"
160 // Retrieval info: CONSTANT: WIDTH_BYTEENA_A NUMERIC "1"
161 // Retrieval info: USED_PORT: address 0 0 5 0 INPUT NODEFVAL "address[4..0]"
162 // Retrieval info: USED_PORT: clock 0 0 0 0 INPUT VCC "clock"
163 // Retrieval info: USED_PORT: data 0 0 8 0 INPUT NODEFVAL "data[7..0]"
164 // Retrieval info: USED_PORT: q 0 0 8 0 OUTPUT NODEFVAL "q[7..0]"
165 // Retrieval info: USED_PORT: wren 0 0 0 0 INPUT NODEFVAL "wren"
166 // Retrieval info: CONNECT: @address_a 0 0 5 0 address 0 0 5 0
167 // Retrieval info: CONNECT: @clock0 0 0 0 0 clock 0 0 0 0
168 // Retrieval info: CONNECT: @data_a 0 0 8 0 data 0 0 8 0
169 // Retrieval info: CONNECT: @wren_a 0 0 0 0 wren 0 0 0 0
170 // Retrieval info: CONNECT: q 0 0 8 0 @q_a 0 0 8 0
171 // Retrieval info: GEN_FILE: TYPE_NORMAL ram32x8.v TRUE
172 // Retrieval info: GEN_FILE: TYPE_NORMAL ram32x8.inc FALSE
173 // Retrieval info: GEN_FILE: TYPE_NORMAL ram32x8.cmp FALSE
174 // Retrieval info: GEN_FILE: TYPE_NORMAL ram32x8.bsf FALSE
175 // Retrieval info: GEN_FILE: TYPE_NORMAL ram32x8_inst.v FALSE
176 // Retrieval info: GEN_FILE: TYPE_NORMAL ram32x8_bb.v FALSE
177 // Retrieval info: LIB_FILE: altera_mf
178

```

```

1 timescale 1ns/1ns
2
3 // Aidan Lee, Aarin Wen
4 // 11/13/2024
5 // EE 371
6 // Lab 4
7
8 // Control module for the binary search task for Lab 4. Is in charge of managing states, bounds of the search
9 // area, etc.
10
11 // utilizes clk input
12 // input reset resets the search (clears the output) and waits for another start signal
13 // input [7:0] A represents the desired value that you want to find inside the RAM
14 // input start starts the algorithm. Waits for this value to go to high before starting
15 // input [7:0] data_out the data at address to_check, received by the datapath module
16 // output found goes high if the value A was found in the ram
17 // output notfound goes high at the end when finished if the value A was not found
18 // output done goes high if algorithm is finished
19 // output to_check tells the datapath module what address to find the value of next
20 // output [4:0] loc represents the address location where the value is found
21
22 module task2_control (reset, clk, A, data_out, start, found, notfound, done, to_check, loc);
23
24     input logic reset, clk, start;
25
26     input logic [7:0] A;
27
28     // Data_out - The data out of the RAM module after feeding it in an address
29     input logic [7:0] data_out;
30
31     output logic found, notfound, done;
32     // The address to check: the middle address between the upper bound and lower bound. 5 bits to match the RAM module
33     output logic [4:0] to_check;
34     output logic [4:0] loc;
35
36     // upper bounds and lower bounds of the binary search. added an extra bit so that it can hold 32
37     logic [5:0] upper_bound, lower_bound;
38
39     // next_bounds - Control signal that reports whether the upper or lower
40     // bounds should be adjusted for the next search. 2 bits long so that 2'b11 can
41     // signal to stop adjusting bounds
42     logic [1:0] next_bounds;
43
44     // control circuit
45     logic [2:0] ps, ns;
46     parameter S1 = 3'b000, S2 = 3'b001, S3 = 3'b010, S4 = 3'b011, S5 = 3'b100;
47
48     // internal status signal to report the value was not found (INTERNAL ONLY)
49     logic change_bounds;
50
51     // state logic
52     always_comb begin
53         case (ps)
54             S1: if (start == 0) ns = S1; // initial state: wait until start signal
55                 else ns = S2;
56             S2: ns = S3; // do algorithm for one clock cycle
57             S3: if (data_out == A || notfound) ns = S5; // decide if algorithm should be repeated or if we are done
58                 else ns = S4;
59             S4: ns = S2; // update bounds
60             S5: if (start == 0) ns = S1; // done state
61                 else ns = S5;
62         endcase
63     end
64
65     // state control ff
66     always_ff @(posedge clk) begin
67         if (reset)
68             ps <= S1;
69         else
70             ps <= ns;
71     end
72
73     // comb logic that assigns control and status signals - prepares what direction
74     // next upper and lower bounds should go to if value not found
75     always_comb begin
76         done = 0; loc = 0; next_bounds = 2'b11;
77         case (ps)
78             S4: begin
79                 if (data_out > A) begin
80                     next_bounds = 0;
81                 end
82                 else if (data_out < A) begin
83                     next_bounds = 1;
84                 end
85             end
86             S5: begin
87                 // edge case: if data not found, report 0
88                 if (!notfound)
89                     loc = to_check;
90
91                 done = 1;
92             end
93             default: begin
94                 done = 0; loc = 0; next_bounds = 2'b11;
95             end
96         endcase
97     end
98
99     // clock logic to make upper and lower bounds assigned on correct clock cycle
100     always_ff @(posedge clk) begin
101         // default case
102         if (reset || start == 0) begin
103             upper_bound <= 32;
104             lower_bound <= 0;
105         end
106         // edge case: when value is at upper bound address 31
107         else if (change_bounds) begin
108             upper_bound <= 33;
109             lower_bound <= 31;
110         end
111         // adjust lower bounds (according to next_bounds)
112         else if (next_bounds == 2'b01) begin
113             upper_bound <= upper_bound;
114             lower_bound <= to_check + 1;
115         end
116         // adjust upper bounds (according to next_bounds)

```

```

115     end else if (next_bounds == 2'b00) begin
116         upper_bound <= to_check + 1;
117         lower_bound <= lower_bound;
118         // otherwise, don't touch the bounds. usually for initial run, or when algo finishes
119     end else begin
120         upper_bound <= upper_bound;
121         lower_bound <= lower_bound;
122     end
123 end
124
125 // calculation to determine whether to check the upper half or lower half for binary search
126 assign to_check = ((upper_bound - lower_bound)/2) + lower_bound - 1;
127 // reports that the correct value was found once finished running algorithm
128 assign found = (data_out == A) && done;
129 // signal to change bounds
130 assign change_bounds = ((upper_bound == 32) && (lower_bound == 31));
131 // signal to check that the value was not found (triggers at the end when finished)
132 assign notfound = ((upper_bound - lower_bound) == 1) && (data_out != A);
133
134 endmodule
135
136 module control_tb ();
137
138     logic reset, clk, start;
139
140     logic [7:0] A;
141
142
143     logic [7:0] data_out;
144
145     logic found, notfound, done;
146
147     logic [4:0] to_check;
148     logic [4:0] loc;
149
150     // Clock logic
151     parameter CLOCK_PERIOD = 5; // Increase clock frequency
152     initial begin
153         clk <= 0;
154         forever #(CLOCK_PERIOD/2) clk <= ~clk; // Forever toggle the clock
155     end
156
157     task2_control dut (.*);
158
159     initial begin
160
161         A <= 8'b00000000; start <= 1'b0; data_out <= 0;
162         reset <= 1; @(posedge clk);
163         @(posedge clk);
164
165         // check not finding it (should try to go down in address
166         start <= 1'b1; reset <= 0; A <= 8'b00000000; data_out <= 8'd15;
167         repeat (8) @(posedge clk);
168
169         reset <= 1; start <= 1'b0; @(posedge clk);
170         @(posedge clk);
171
172         // check finding it
173         start <= 1'b1; reset <= 0; A <= 8'b00000000; data_out <= 8'b0;
174         repeat (8) @(posedge clk);
175
176
177         $stop;
178     end
179 end
180
181 endmodule

```

## 9) task2\_datapath.sv



```

1  `timescale 1ns/1ns
2
3  // Aidan Lee, Aarin Wen
4  // 11/13/2024
5  // EE 371
6  // Lab 4
7  //
8  // Datapath module for the binary search task for Lab 4. Is in charge of storing memory,
9  // and telling the control module what value is at every address it looks for.
10 //
11 // utilizes clk input
12 // input to_check      tells the datapath module what address to find the value of next
13 // output [7:0] data_out represents the address location where the value is found
14
15 module task2_datapath (to_check, clk, data_out);
16
17     input logic [4:0] to_check;
18     input logic clk;
19     output logic [7:0] data_out;
20
21     // 32x8 ram module, instantiated using the built in methods taught in lab 2
22     // takes in a 5bit address to check the value currently in that address to find the desired value
23     // takes in a clock input
24     // takes in data (doesn't matter. never reading)
25     // takes in wren as a write enable (which is always 0, never going to matter)
26     // outputs 8bit data_out to reveal what's in the ram at the given address
27     ram32x8 ram (.address(to_check), .clock(clk), .data(1'b1), .wren(1'b0), .q(data_out));
28
29 endmodule
30
31 module datapath_tb ();
32
33     logic [4:0] to_check;
34     logic clk;
35     logic [7:0] data_out;
36
37     // Clock logic
38     parameter CLOCK_PERIOD = 5; // Increase clock frequency
39     initial begin
40         clk <= 0;
41         forever #(CLOCK_PERIOD/2) clk <= ~clk; // Forever toggle the clock
42     end
43
44     task2_datapath dut (.*);
45
46     initial begin
47         // check whats in every address
48         for (int i = 0; i < 32; i++) begin
49             to_check = i;
50             @(posedge clk);
51             end;
52             $stop;
53         end
54     end
55
56 endmodule

```